

## **IMPLEMENTATION OF FULL ADDER AND FULL SUBTRACTOR USING LOGIC GATES**

### **Objective:**

To realize the operation of adder and subtractor circuit using basic logic gates.

### **LIST OF MAJOR EQUIPMENTS:**

<b>SI No.</b>	<b>Name</b>	<b>Manufacturer</b>	<b>Model No</b>	<b>Specification</b>
1.	Power Supply	ELNOVA/ Aplab	E-61	S1:0-30V, S2:0-2V, S3:5V,5A
2.	Logic Probe	Made in Taiwan	Model-625	50 MHz freq. range

### **Theory:**

A combinational circuit that performs the addition of 2 bits is called the half adder. One that performs the addition of three bits is called a full adder.

A half adder has 2 inputs and 2 outputs. The output variables produce the sum and carry.

In full adder two input variables A and B represents the two significant bits to be added. The third input C represents the carry from the previous lower significant position. It has two outputs sum and carry.

A half sub tractor is a combinational circuit that subtracts two bits. It has two inputs and two outputs. The output variables produce difference and borrow. A full subtractor is a combinational circuit that performs subtraction between two bits taking into account one may have been borrowed by a lower significant stage. It has three inputs and two outputs.

### **TRUTH TABLE FOR HALF ADDER AND HALF SUBTRACTOR:**

HALF ADDER  
SUBTRACTOR

HALF

A	B	SUM	CARRY
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

A	B	DIFF	Borrow
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

### **TRUTH TABLE FOR FULL ADDER AND FULL SUBTRACTOR:**

### **OBSERVATION TABLE FOR HALF ADDER AND HALF**

A	B	C	SUM	CARRY	DIFF	BORROW
0	0	0	0	0	0	0
0	0	1	1	0	1	1
0	1	0	1	0	1	1
0	1	1	0	1	0	1
1	0	0	1	0	1	0
1	0	1	0	1	0	0
1	1	0	0	1	0	0
1	1	1	1	1	1	1

### **SUBTRACTOR:**

#### **HALF ADDER**

A	B	SUM	CARRY
L	L	L	L
L	H	H	L
H	L	H	L
H	H	L	H

#### **HALF SUBTRACTOR**

A	B	DIFF	Borrow
L	L	L	L
L	H	H	H
H	L	H	L
H	H	L	L

### **OBSERVATION TABLE FOR FULL ADDER AND FULL SUBTRACTOR:**


#### **FULL ADDER**

A	B	C	SUM	CARRY
L	L	L	L	L
L	L	H	H	L
L	H	L	H	L
L	H	H	L	H
H	L	L	H	L
H	L	H	L	H
H	H	L	L	H
H	H	H	H	H

### **FULL SUBTRACTOR**


A	B	Cin	DIFF	Borrow
L	L	L	L	L
L	L	H	H	H
L	H	L	H	H
L	H	H	L	H
H	L	L	H	L
H	L	H	L	L
H	H	L	L	L
H	H	H	H	H

### **CIRCUIT DIAGRAM**

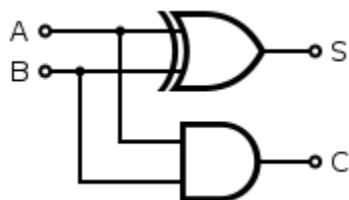

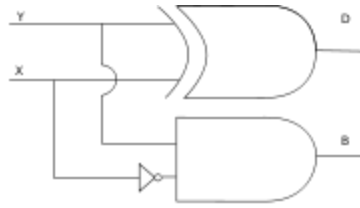
### HALF ADDER

NOTE: give the Boolean expression for SUM and CARRY by yourself.



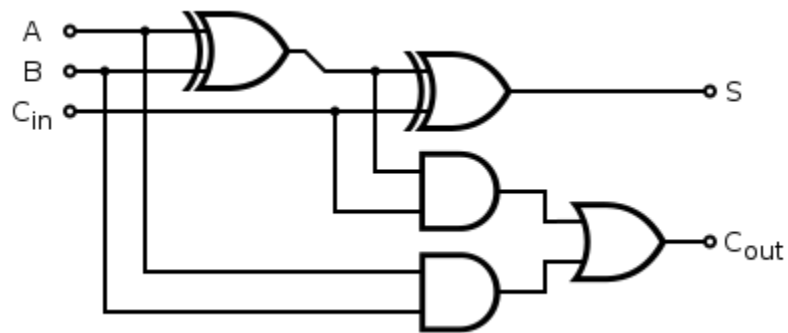
### HALF SUBTRACTOR

NOTE: give the Boolean expression for DIFFERENCE and BORROW by yourself.


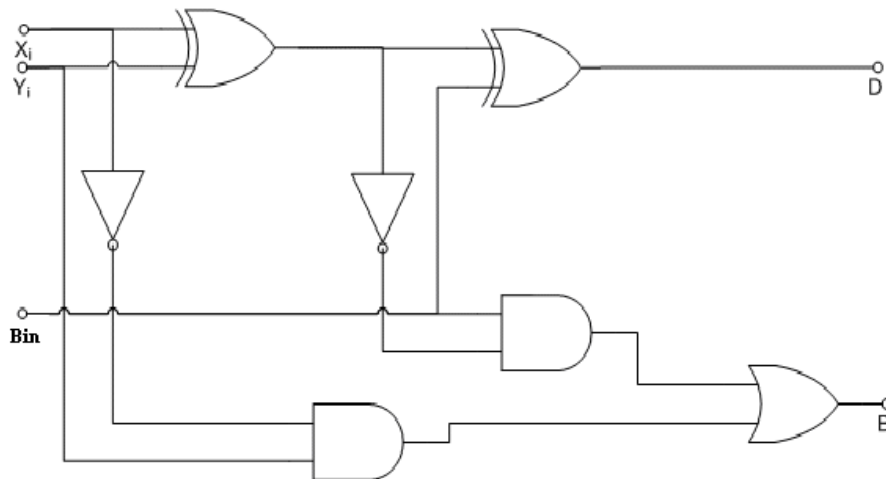
### FULL ADDER

NOTE: give the Boolean expression for SUM and CARRY by yourself.




### FULL SUBTRACTOR


NOTE: give the Boolean expression for DIFFERENCE and BORROW by yourself.




# CIRCUIT DIAGRAM

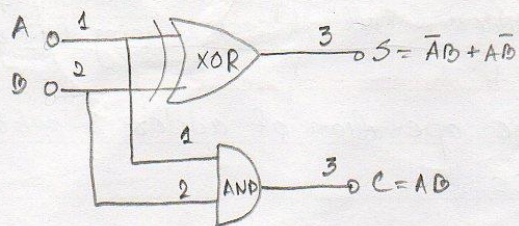


HALF ADDER.

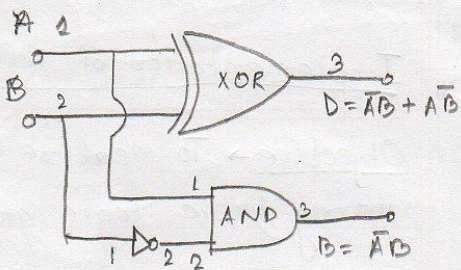

HALF SUBTRACTOR.

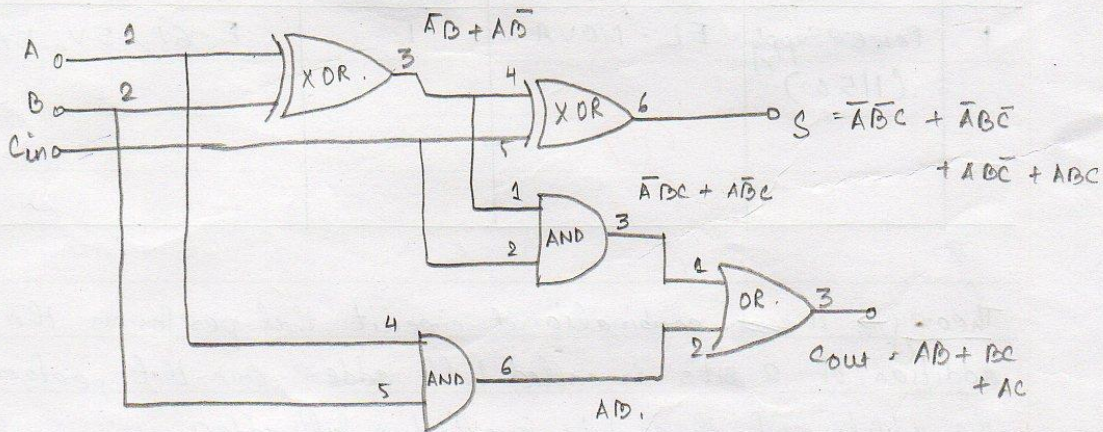

Full Adder.

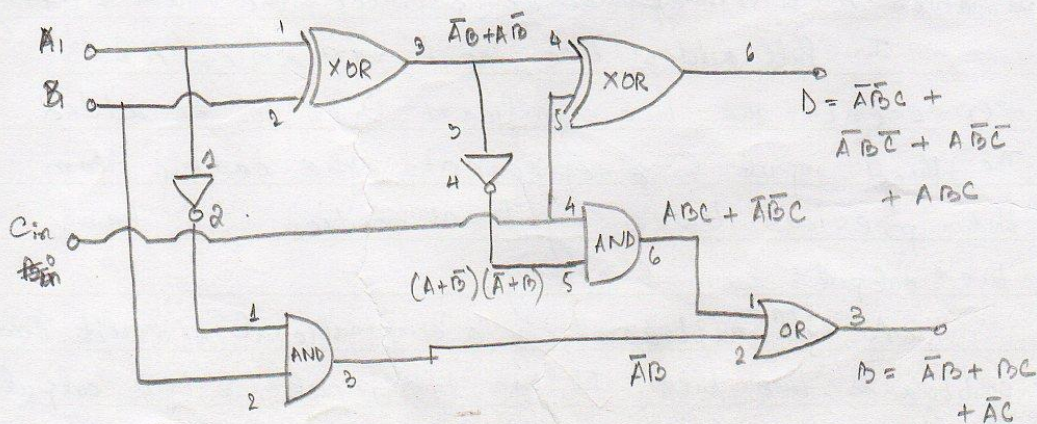

Full Subtractor

**For Half Adder**

**K-Map for SUM:**

A \ B	00	01
	00	01
00		1
01	1	

$$\text{SUM} = A'B + AB'$$

**K-Map for CARRY:**

A \ B	00	01
	00	01
00		
01		1

$$\text{CARRY} = AB$$

**For Full Adder**

**K-Map for SUM:**

A \ BC	00	01	11	10
	00	01	11	10
0		1		1
1	1		1	

$$\text{SUM} = A'B'C + A'BC' + ABC' + ABC$$

**K-Map for CARRY:**

		BC			
		00	01	11	10
A	0			1	
	1		1	1	1

$$\text{CARRY} = AB + BC + AC$$

**For Half Subtractor**

**K-Map for DIFFERENCE:**

		B	
		00	01
A	00		1
	01	1	

$$\text{DIFFERENCE} = A'B + AB'$$

**K-Map for BORROW:**

		B	
		00	01
A	00		1
	01		

$$\text{BORROW} = A'B$$



### For full Subtractor

**K-Map for Difference:**

A \ BC				
	00	01	11	10
0		1		1
1	1		1	

$$\text{Difference} = A'B'C + A'BC' + AB'C' + ABC$$

**K-Map for Borrow:**

A \ BC				
	00	01	11	10
0		1	1	1
1			1	

$$\text{Borrow} = A'B + BC + A'C$$

### CONCLUSION:

NOTE: Here are some Questions. You need not write the questions , You only write the answers

1. Can we construct a full adder and full subtractor circuit using universal gates.
2. What are the uses of full adder and full subtractor circuit