

### **Experiment No. 3**

**TITLE** :- Construction of simple decoder & multiplexer circuits using logic gates.

**Object** :- To construct a simple decoder & multiplexer circuit using logic gates & to show its operation.

**List of equipments** :-


Sl No.	Name	Manufacturer	Model No.	Specification
1	Regulated DC power Supply	ELNOVA	E-61	5V, 5A
2	Logic Probe	Taiwan Make	Model-625	50MHz Frequency Range


**Theory** :-

A decoder is a combinational logic circuit that converts binary information from 'n' input lines to a maximum of  $2^n$  unique output lines.

Multiplexing is the process of transmitting a large number of information over a single line. A multiplexer is a combinational logic circuit which has  $2^n$  input line, n select and only one output line. The selection of a particular input line is controlled by the set of select line. It determines which inputs will go to the output.

**Circuit diagram**

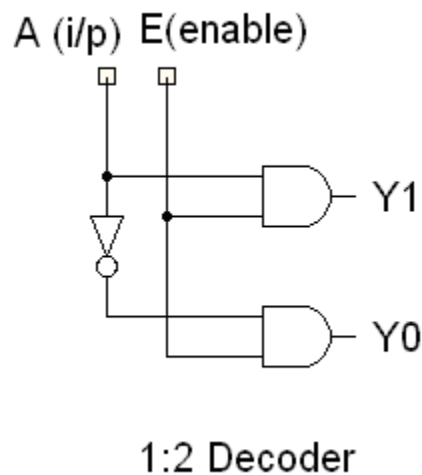

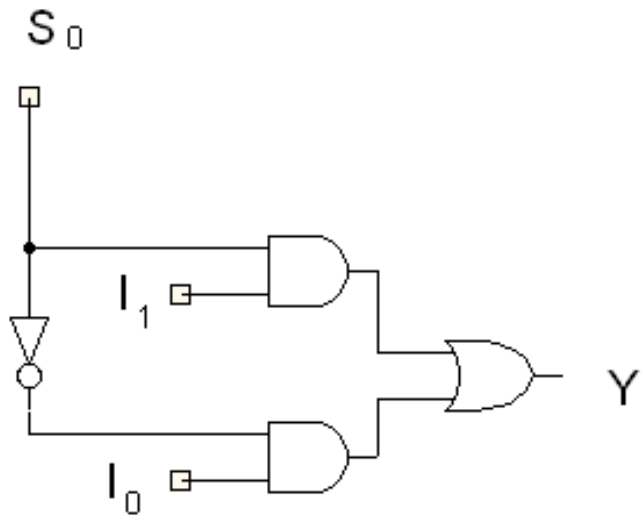

## 2:1 Multiplexer

Truth table :-

1:2 decoder

Inputs		Enable	Outputs	
A		E	$Y_0$	$Y_1$
X		0	0	0
0		1	1	0
1		1	0	1

2:1 MUX

Inputs		Select line	Output
$I_0$	$I_1$	$S_0$	Y
X	X	0	$I_0$
X	X	1	$I_1$

### Observation table

#### 1:2 Decoder

Input		Enable	Output	
A	L	E	$Y_0$	$Y_1$
L	L	L	L	L
H	L	L	L	L
L	H	H	H	L
H	H	H	L	H

#### 2:1 Multiplexer

Input		Select line	Output
$I_0$	$I_1$	$S_0$	Y
L	L	L	L
L	H	L	L
H	L	L	H
H	H	L	H
L	L	H	L
L	H	H	H
H	L	H	L
H	H	H	H

### CONCLUSION:

NOTE: Here are some Questions. You need not write the questions, You only write the answers

1. What are the use of DECODER and MULTIPLEXER circuit in practical?